

### Question 3.

A circuit equivalent to the given one is shown in Fig. 3. In a steady state (the capacitors are completely charged already) the same current  $I$  flows through all the resistors in the closed circuit A B F G H D A. From the Kirchoff's second rule we obtain:

$$(3.1) \quad I = \frac{E_4 - E_1}{4R}.$$

Next we apply this rule for the circuit ABCDA:

$$(3.2) \quad V_1 + IR = E_2 - E_1,$$

where  $V_1$  is the potential difference across the capacitor  $C_1$ . By using the expression (3.1) for  $I$ , and the equation (3.2) we obtain:

$$(3.3) \quad V_1 = E_2 - E_1 - \frac{E_4 - E_1}{4} = 1 \text{ V}.$$

Similarly, we obtain the potential differences  $V_2$  and  $V_4$  across the capacitors  $C_2$  and  $C_4$  by considering circuits BFGCB and FGHEF:

$$(3.4) \quad V_2 = E_4 - E_2 - \frac{E_4 - E_1}{4} = 5 \text{ V},$$

$$(3.5) \quad V_4 = E_4 - E_3 - \frac{E_4 - E_1}{4} = 1 \text{ V}.$$

Finally, the voltage  $V_3$  across  $C_3$  is found by applying the Kirchoff's rule for the outermost circuit EHD A H:

$$(3.6) \quad V_3 = E_3 - E_1 - \frac{E_4 - E_1}{4} = 5 \text{ V}.$$

The total energy of the capacitors is expressed by the formula:

$$(3.7) \quad W = \frac{C}{2} (V_1^2 + V_2^2 + V_3^2 + V_4^2) = 26 \mu\text{J}.$$

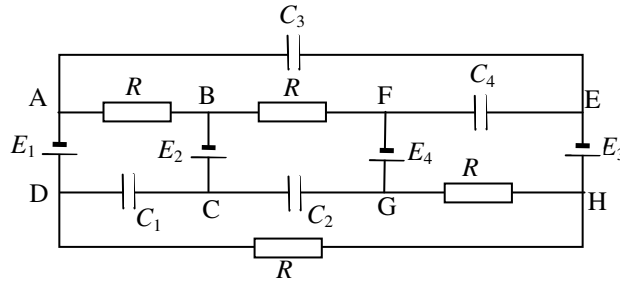


Fig. 3

When points B and H are short connected the same electric current  $I'$  flows through the resistors in the BFGH circuit. It can be calculated, again by means of the Kirchoff's rule, that:

$$(3.8) \quad I' = \frac{E_4}{2R}.$$

The new steady-state voltage on  $C_2$  is found by considering the BFGCB circuit:

$$(3.9) \quad V'_2 + I'R = E_4 - E_2$$

or finally:

$$(3.10) \quad V_2' = \frac{E_4}{2} - E_2 = 0 \text{ V.}$$

Therefore the charge  $q_2'$  on  $C_2$  in the new steady state is zero.