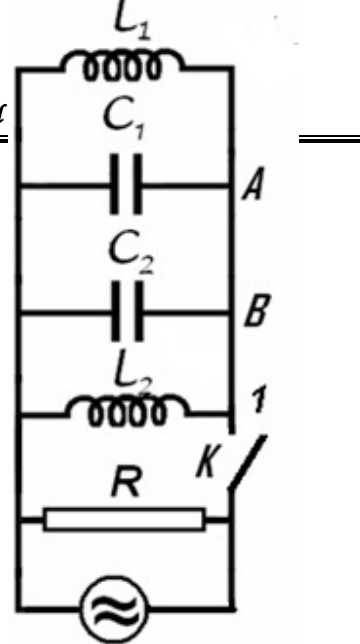


**Electricity – Problem II (8 points)**

**Different kind of oscillation**

Let's consider the electric circuit in the figure, for which  $L_1 = 10 \text{ mH}$ ,  $L_2 = 20 \text{ mH}$ ,  $C_1 = 10 \text{ nF}$ ,  $C_2 = 5 \text{ nF}$  and  $R = 100 \text{ k}\Omega$ . The switch  $K$  being closed the circuit is coupled with a source of alternating current. The current furnished by the source has constant intensity while the frequency of the current may be varied.

- a. Find the ratio of frequency  $f_m$  for which the active power in circuit has the maximum value  $P_m$  and the frequency difference  $\Delta f = f_+ - f_-$  of the frequencies  $f_+$  and  $f_-$  for which the active power in the circuit is half of the maximum power  $P_m$ .



The switch  $K$  is now open. In the moment  $t_0$  immediately after the switch is open the intensities of the currents in the coils  $L_1$  and  $L_2$  are  $i_{01} = 0,1 \text{ A}$  and  $i_{02} = 0,2 \text{ A}$  ( $L_1$  the currents flow as in the figure); at the same moment, the potential difference on the capacitor with capacity  $C_1$  is  $u_0 = 40 \text{ V}$ :

- b. Calculate the frequency of electromagnetic oscillation in  $L_1 C_1 C_2 L_2$  circuit;
- c. Determine the intensity of the electric current in the  $AB$  conductor;
- d. Calculate the amplitude of the oscillation of the intensity of electric current in the coil  $L_1$ .

*Neglect the mutual induction of the coils, and the electric resistance of the conductors. Neglect the fast transition phenomena occurring when the switch is closed or opened.*

