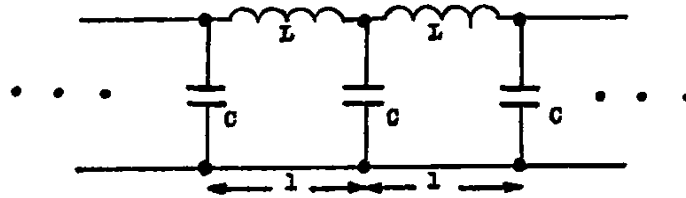


Problem 3: Infinite LC-grid

When sine waves propagate in an infinite LC-grid (see the figure below) the phase of the ac-voltage across two successive capacitors differs by Φ .



- Determine how Φ depends on ω , L and C (ω is the angular frequency of the sine wave).
- Determine the velocity of propagation of the waves if the length of each unit is ℓ .
- State under what conditions the propagation velocity of the waves is almost independent of ω . Determine the velocity in this case.
- Suggest a simple mechanical model which is an analogue to the above circuit and derive equations which establish the validity of your model.

Formulae:

$$\cos \alpha - \cos \beta = -2 \cdot \sin \left(\frac{\alpha + \beta}{2} \right) \cdot \sin \left(\frac{\alpha - \beta}{2} \right)$$

$$\sin \alpha - \sin \beta = 2 \cdot \cos \left(\frac{\alpha + \beta}{2} \right) \cdot \sin \left(\frac{\alpha - \beta}{2} \right)$$